
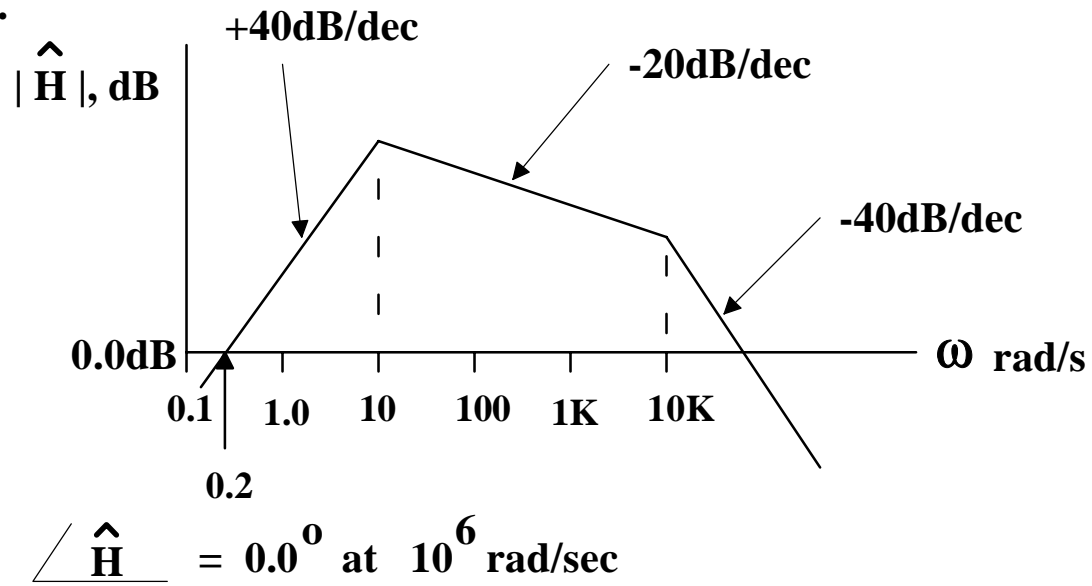


1.

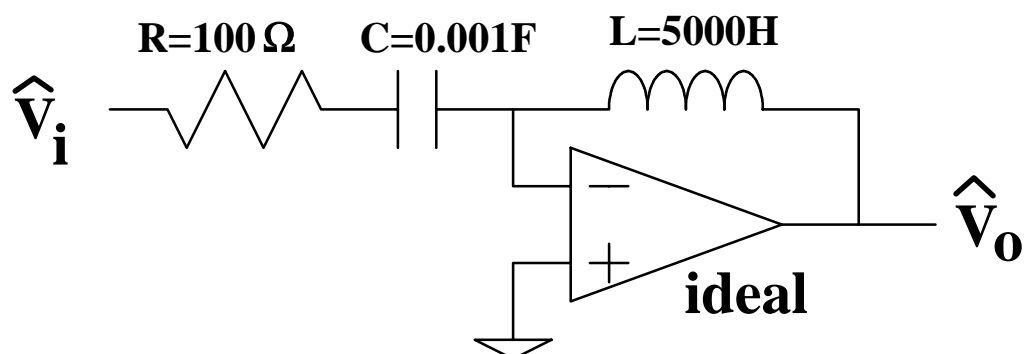

Determine $\hat{H}(j\omega)$ from the Bode plot shown above. Note that the angle at high frequency is given.

2.




Determine the transfer function, $\hat{H}(j\omega)$, for the ideal op amp circuit shown above.

3. For the following transfer function: put it into standard form, evaluate at appropriate frequencies, and make an approximate graph of $|\hat{H}|$, dB versus $\log(\omega)$.

$$\hat{H} = \frac{+10^5 \omega^2}{(1+10j\omega)(10^4 - \omega^2 + j\omega)}$$

4.

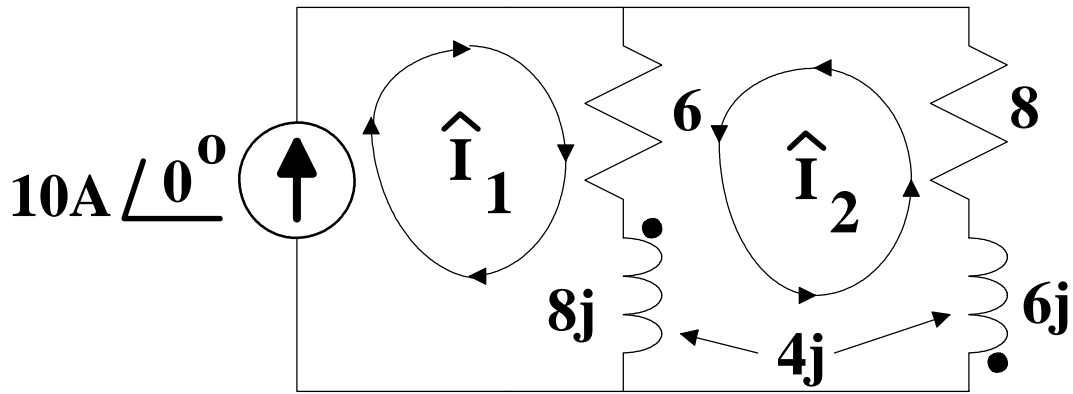


(a.) Draw the equivalent of the circuit shown above. **NOTE:** that the mesh current

\hat{I}_1 flows clockwise, but the current \hat{I}_2 flows counterclockwise.

(b.) Write down the set of equations required to solve for \hat{I}_2 , but do not solve.

5.

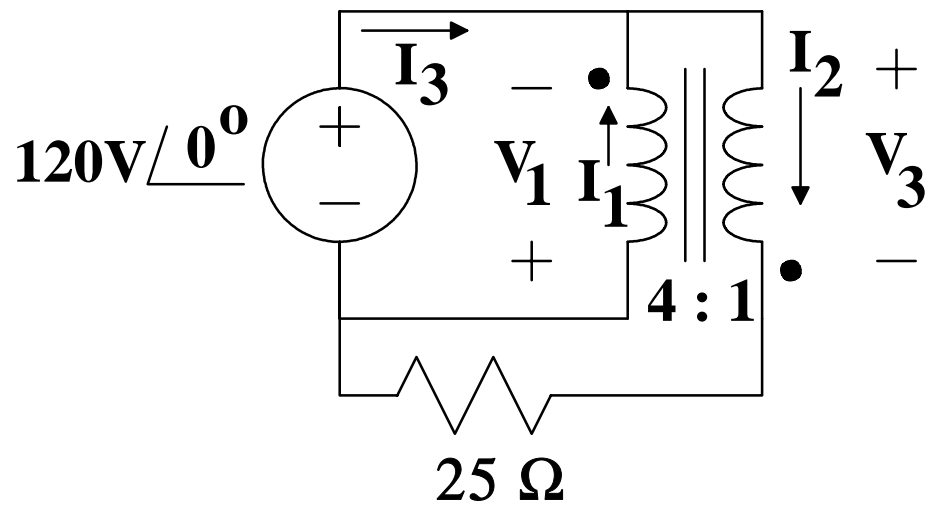


For the ideal transformer circuit shown above, write down the set of equations that would allow one to solve for the 5 labeled unknowns. Do not solve the equations.

6. A balanced three phase load requires 480 kW (total for all three phases) at a leading power factor of 0.80. The load is fed from a line having an impedance of $(0.005 + j0.025)\Omega/\phi$. The line voltage at the load, $|\hat{V}_{AB}|$, is 600V.


- (a.) Determine the magnitude of the line voltage at the sending end of the line.
- (b.) Calculate the power factor at the sending end of the line.

7.

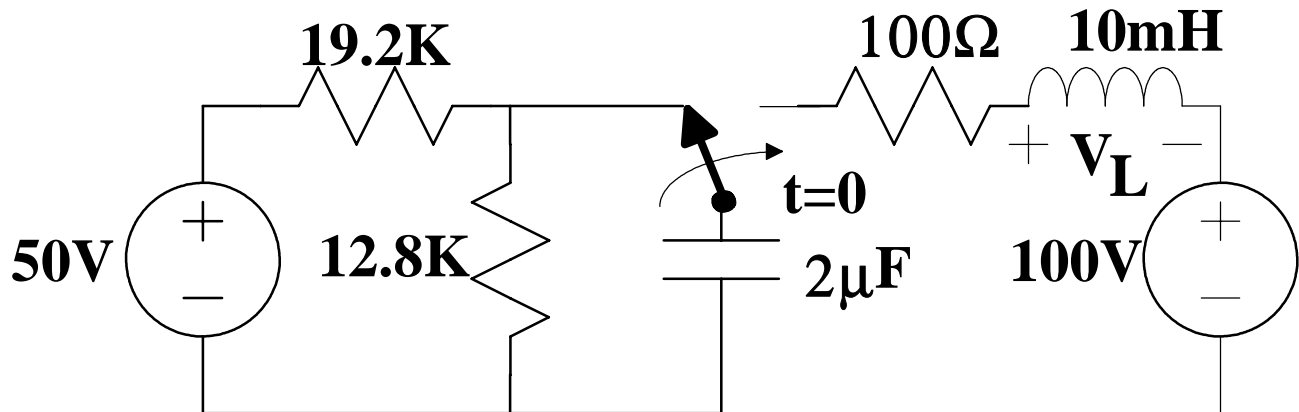

The switch has been at the left contact for a very long time. At $t=0$, the switch is flipped to the right contact. Determine $V_L(t)$ for $t \geq 0$.

8.

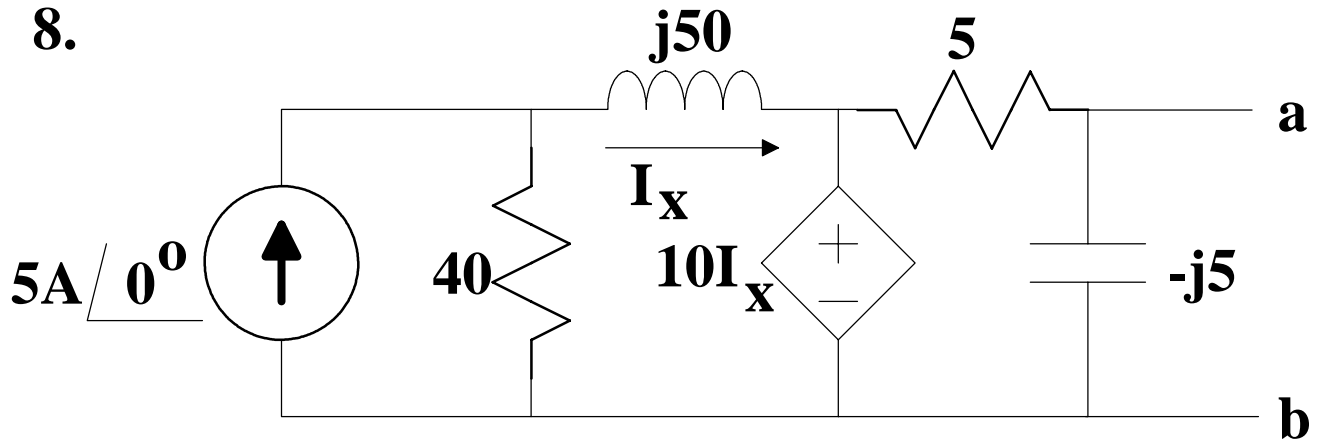

Write down the complete set of equations that would allow one to solve for the Thevenin impedance between terminals a and b, of the circuit shown above. Do not solve the equations.